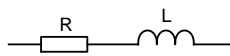


$$z = U_m \cdot e^{j\varphi} = U_m \cdot (\cos \varphi + j \cdot \sin \varphi)$$

$$z = a + j \cdot b$$

$$|z| = \sqrt{a^2 + b^2}$$

$$|e^{j\varphi}| = \sqrt{\cos^2 \varphi + \sin^2 \varphi} = 1$$




$$\hat{Z}_R + \hat{Z}_L = \frac{R}{a} + j \frac{\omega L}{b}$$

$$\operatorname{tg} \varphi = \frac{b}{a} \Rightarrow \varphi = \operatorname{arctg} \frac{b}{a}$$

$$\hat{I} = \frac{\hat{U}}{\hat{Z}} = \hat{U} \cdot \hat{Y}$$

$$\Psi = -\varphi$$

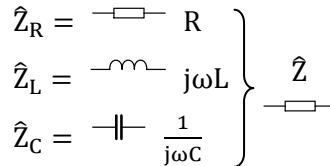

$$\hat{U} = \hat{Z} \cdot \hat{I}$$


$$\hat{I} = |I_m| \cdot e^{j0}$$

$$\hat{Z} = |\hat{Z}| \cdot e^{j\varphi}$$



$$\hat{U} = U_m \cdot e^{j\alpha} = |\hat{Z}| \cdot e^{j\varphi} \cdot |I_m| \cdot e^{j0}$$

$$\hat{U} = U_m \cdot e^{j\alpha} = |\hat{Z}| |I_m| \cdot e^{j\varphi}$$

$$\alpha = \varphi$$

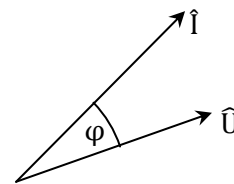

RL obvod

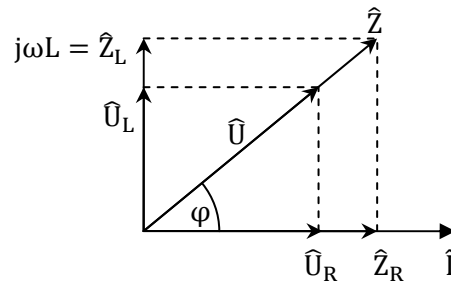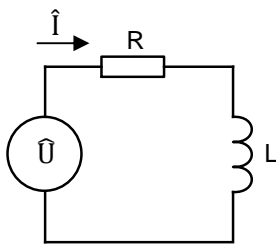

$$|\hat{U}| = \sqrt{|\hat{U}_R|^2 + |\hat{U}_L|^2} = \frac{\sqrt{(\omega L)^2 + R^2} \cdot |\hat{I}|}{|\hat{Z}|}$$

$$\hat{U} = \hat{U}_R + \hat{U}_L = R \cdot \hat{I} + j\omega L \cdot \hat{I} = (R + j\omega L) \cdot \hat{I}$$

$$|\hat{U}| = |\hat{I}| \cdot |R + j\omega L| = |\hat{I}| \cdot \sqrt{R^2 + (\omega L)^2}$$

$$\hat{U}_R = R \cdot \hat{I}$$



$$\hat{U}_L = j\omega L \cdot \hat{I}$$

$$|U_L| = |j\omega L| \cdot |\hat{I}| = \omega L \cdot |\hat{I}|$$

$$|U_R| = R \cdot |\hat{I}|$$

$$\operatorname{tg} \varphi = \frac{\omega L}{R}$$

RC obvod

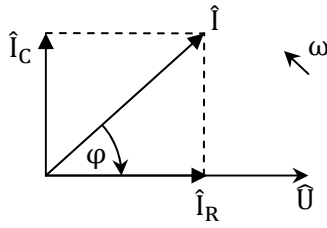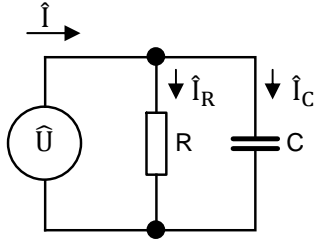

$$Y_R = \frac{1}{R}$$

$$Y_C = j\omega C$$

$$Y_L = \frac{1}{j\omega L}$$




$$\hat{I} = \hat{I}_R + \hat{I}_C \quad \hat{I} = \hat{Y} \cdot \hat{U}$$

$$\hat{U} = \hat{Z} \cdot \hat{I}$$

$$\hat{Z} = \frac{Z_R \cdot Z_C}{Z_R + Z_C} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \cdot j\omega C = \frac{R}{Rj\omega C + 1} \cdot \frac{1 - j\omega RC}{1 - j\omega RC} = \frac{R}{1 + \omega^2 R^2 C^2} + j \cdot \frac{R}{1 + \omega^2 R^2 C^2}$$

$$\hat{Z} = \underbrace{R}_{\text{rezistance}} + j \cdot \underbrace{X}_{\text{reaktance}}$$
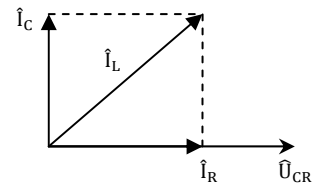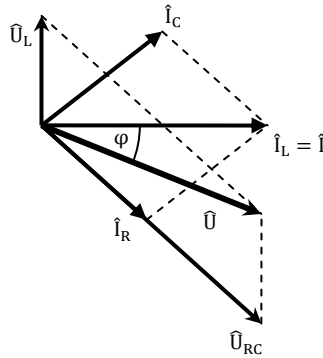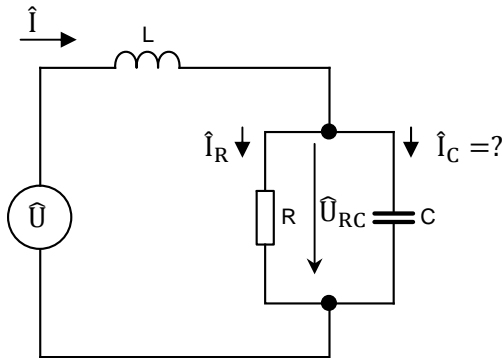
$$\hat{Y} = \underbrace{G}_{\text{konduktance}} + j \cdot \underbrace{B}_{\text{susceptance}}$$



$$\hat{I}_C = \frac{\hat{U}_{RC}}{\hat{Z}_C} = \frac{\hat{U}_{RC}}{\frac{1}{j\omega C}} \quad \hat{Z}_{RC} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$\hat{U}_{RC} = \hat{U} \cdot \frac{\hat{Z}_{RC}}{\hat{Z}_L + \hat{Z}_{RC}} = \hat{U} \cdot \frac{\frac{R}{j\omega C}}{R + \frac{1}{j\omega C}} = \dots = a + j \cdot b = \frac{\sqrt{a^2 + b^2}}{|\hat{I}_C|} \cdot e^{j \cdot \text{artg} \frac{b}{a}}$$

Výkon střídavého proudu


$P = U \cdot I$ - stejnosměrné proudy

$$u = U_m \cdot \sin(\omega t + \varphi)$$

$$i = I_m \cdot \sin(\omega t)$$

$$\left(\begin{array}{l} \sin(x + y) = \sin x \cdot \cos y + \cos x \cdot \sin y \\ \sin 2x = 2 \cdot \sin x \cdot \cos x \\ \cos 2x = \cos^2 x - \sin^2 x \end{array} \right)$$
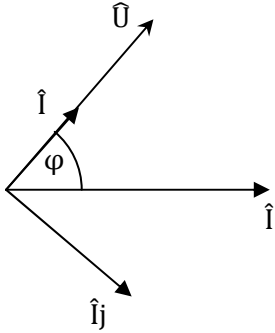
$$p = u(t) \cdot i(t) = U_m \cdot I_m \cdot \sin(\omega t + \varphi) \cdot \sin(\omega t) = U_m \cdot I_m \cdot (\sin(\omega t) \cdot \cos \varphi + \cos(\omega t) \cdot \sin \varphi) \cdot \sin \omega t = \\ = \frac{U_m \cdot I_m}{2} \cdot (\cos \varphi \cdot (1 - \cos(2 \cdot \omega t)) + \sin \varphi \cdot \sin(2 \cdot \omega t))$$



$$P = \frac{1}{T} \cdot \int_0^T p(t) \cdot dt = \dots = \frac{U_m \cdot I_m}{2} \cdot \cos \varphi = \frac{U_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cdot \cos \varphi = U \cdot I \cdot \cos \varphi$$

$$\hat{U}_{\varphi_1} \cdot \hat{I}_{\varphi_2} = U_m \cdot I_m \cdot e^{j \cdot \varphi_1} \cdot e^{j \cdot \varphi_2} = U_m \cdot I_m \cdot e^{j \cdot (\varphi_1 + \varphi_2)}$$



$$\hat{U} \cdot \hat{I}^* = U \cdot I \cdot e^{j \cdot \varphi_1} \cdot e^{-j \cdot \varphi_2} = U \cdot I \cdot e^{j \cdot (\varphi_1 - \varphi_2)} = U \cdot I \cdot (\cos \varphi + j \cdot \sin \varphi)$$

↙ komplexně sdružené

Re { $\hat{U} \cdot \hat{I}^*$ } – činný výkon


Im { $\hat{U} \cdot \hat{I}^*$ } – jalový výkon

Střední hodnota proudu

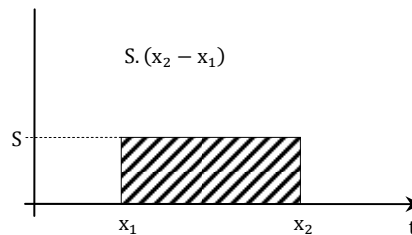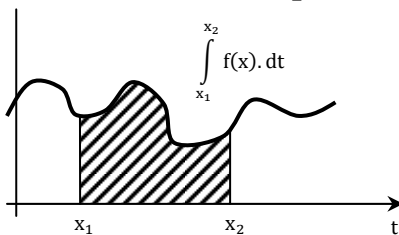


$$\int_{t_1}^{t_2} f(x) \cdot dt = S \cdot (x_2 - x_1)$$

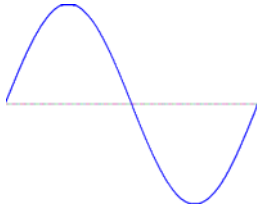
$$\frac{1}{x_2 - x_1} \cdot \int_{x_1}^{x_2} f(x) \cdot dt = S$$


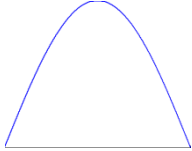
$$U_{ST\check{R}} = \frac{1}{T} \cdot \int_0^T U_m \cdot \sin \omega t \cdot dt = \frac{U_m}{T} \cdot \int_0^T \sin \frac{2\pi}{T} t \cdot dt = \frac{U_m}{T} \cdot \left[-\cos \frac{2\pi}{T} t \right]_0^T \cdot \frac{T}{2\pi} = \frac{U_m}{2\pi} \cdot (-1 + 1) = 0$$


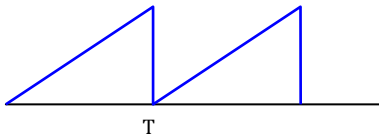
$$U_{ST\check{R}} = \frac{1}{\frac{T}{2}} \cdot \int_0^{\frac{T}{2}} U_m \cdot \sin \omega t \cdot dt = \frac{2}{T} \cdot U_m \cdot \left[-\cos \frac{2\pi}{T} t \right]_0^{\frac{T}{2}} \cdot \frac{T}{2\pi} = \frac{U_m}{\pi} (1 + 1) = \frac{2}{\pi} \cdot U_m$$



$$u(t) = \frac{U_m}{T} t$$


$$U_{ST\check{R}} = \frac{1}{T} \cdot \int_0^T f(t) \cdot dt = \frac{1}{T} \cdot \int_0^T \frac{U_m}{T} t \cdot dt = \frac{U_m}{T^2} \cdot \int_0^T t \cdot dt = \frac{U_m}{T^2} \cdot \left[\frac{t^2}{2} \right]_0^T = \frac{U_m}{2}$$

Efektivní hodnota


$$U_{ef} \cdot I_{ef} \cdot T = \int_0^T u(t) \cdot i(t) \cdot dt$$

Rezonance

Napětíová

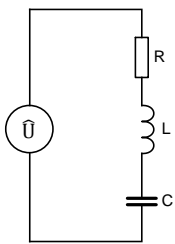
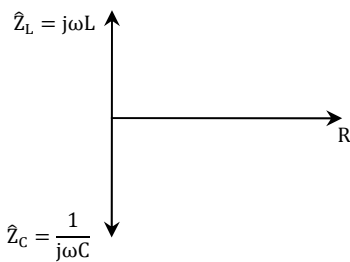
$$\hat{Z} = R + j\omega L + \frac{1}{j\omega C} = R + j \cdot \underbrace{\left(\omega L - \frac{1}{\omega C} \right)}_{=0}$$




$$\omega L - \frac{1}{\omega C} = 0$$

$$\omega L = \frac{1}{\omega C}$$


$$\omega^2 LC = 1$$

$$\omega = \frac{1}{\sqrt{LC}} \Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$
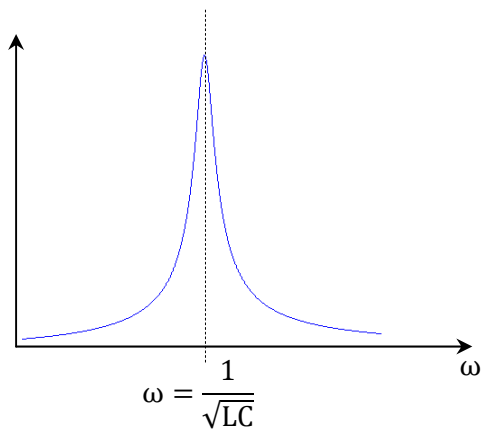
$$\hat{I} = \frac{\hat{U}}{R + j \cdot \left(\omega L - \frac{1}{\omega C} \right)}$$



Proudová

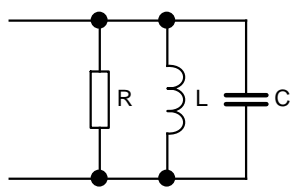

$$Y = G + j\omega C - j \cdot \frac{1}{\omega L} = G + j \cdot \left(\omega C - \frac{1}{\omega L} \right)$$

$$\omega_r = \frac{1}{\sqrt{LC}}$$